

PHYS 1P22/92  
Prof. Barak Shoshany  
Spring 2024


21. Circuits & DC  
Instruments

# 21.1 Resistors in Series and Parallel

---
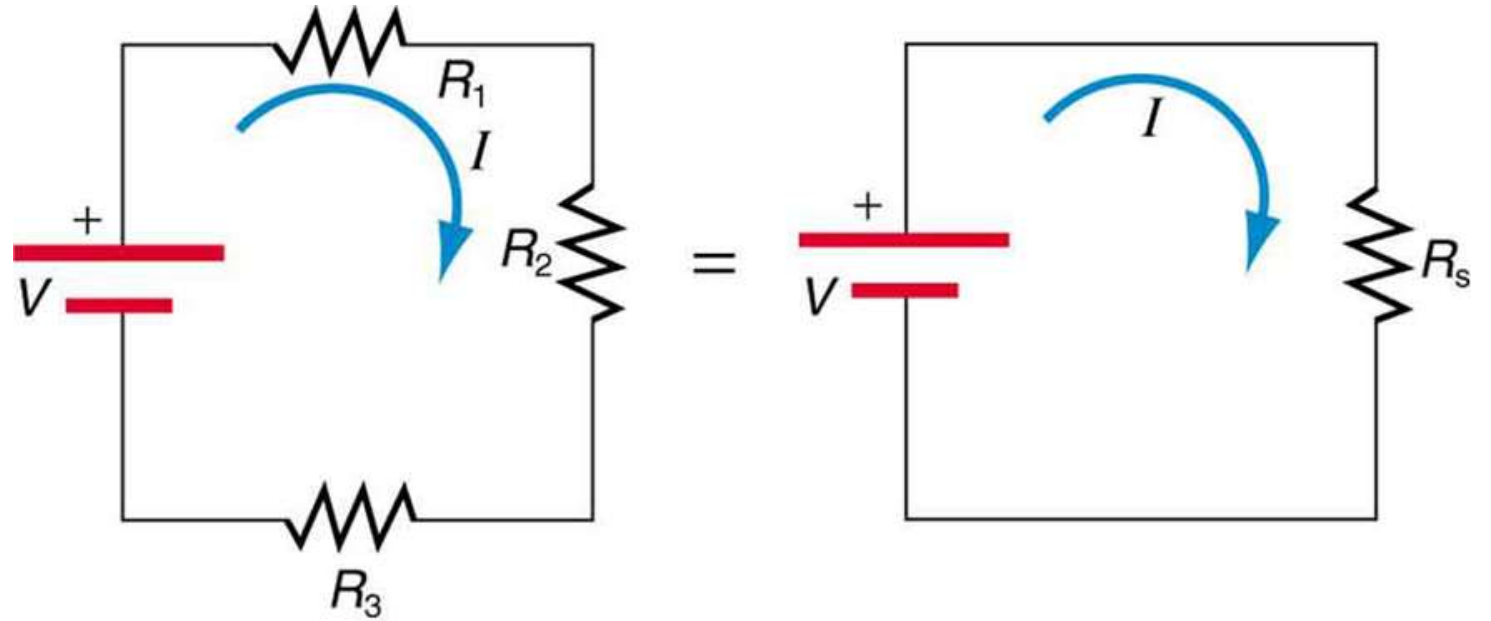
# Series

From conservation of energy: potential energy is  $qV$ , so  $\sum_i qV_i$  must be conserved.



$$V = IR$$


$$V_S = V_1 + V_2 + V_3 = \sum_i V_i$$

$$IR_S = IR_1 + IR_2 + IR_3 = I \sum_i R_i$$

$$R_S = R_1 + R_2 + R_3 = \sum_i R_i$$

Note: each  $R_i$  gets same  $I$  but different  $V_i$ .

# Parallel

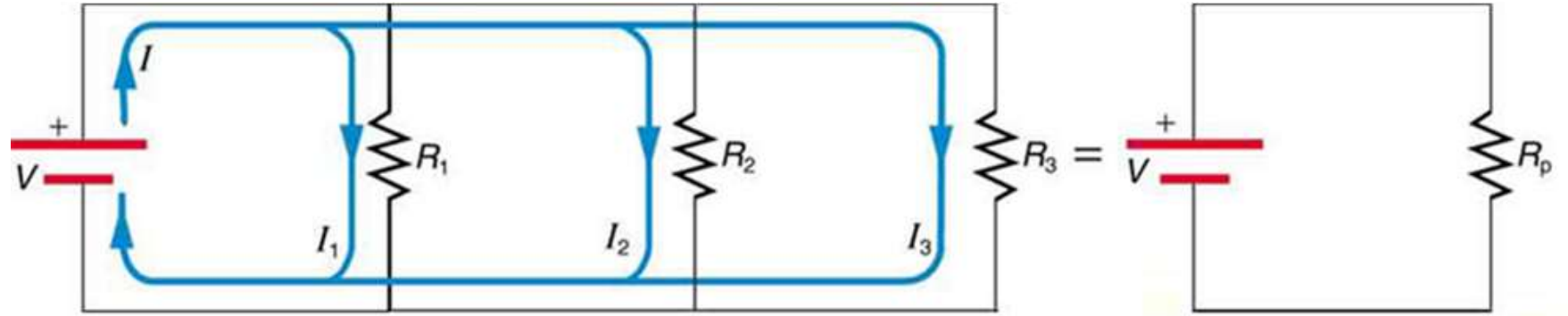

$$I = \frac{V}{R}$$



$$I_P = I_1 + I_2 + I_3 = \sum_i I_i$$



$$\frac{V}{R_P} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \sum_i \frac{1}{R_i}$$




$$R_P = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\sum_i \frac{1}{R_i}}$$



$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \sum_i \frac{1}{R_i}$$

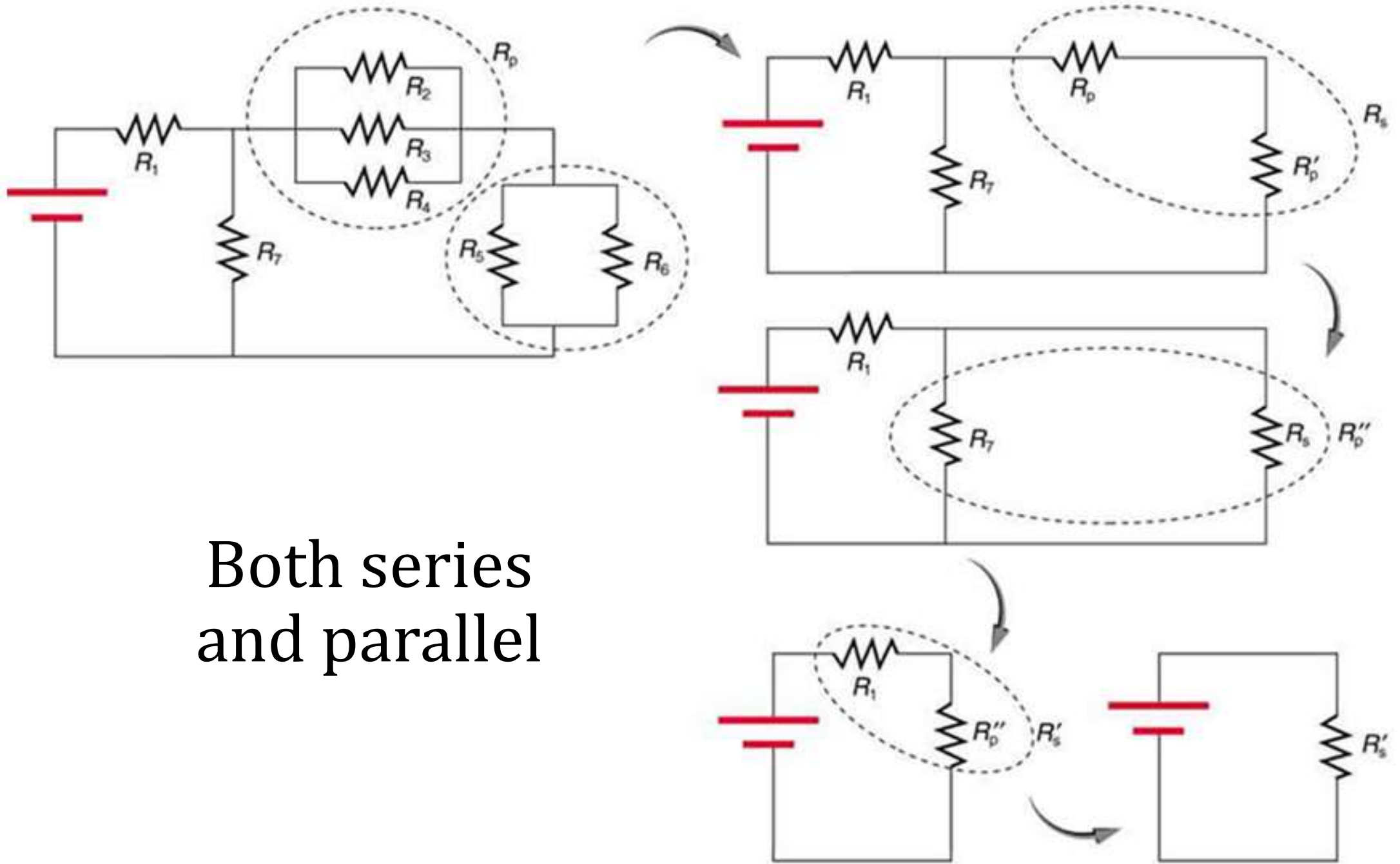Note: each  $R_i$  gets same  $V$  but different  $I_i$ .



Both series  
and parallel

# Capacitors vs. resistors

- Opposite relations:

$$\frac{1}{C_S} = \sum_i \frac{1}{C_i}$$

$$C_P = \sum_i C_i$$

vs.

$$R_S = \sum_i R_i$$

$$\frac{1}{R_P} = \sum_i \frac{1}{R_i}$$

(This is the only section we  
will learn from this chapter.)